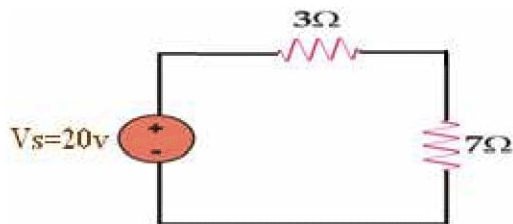


**Question No: 4 ( Marks: 1 ) – Please choose one**

Using voltage divider in the figure below Voltage drop across  $3\Omega$  will be



► 20v

► 14v


► 6v

$$V = \frac{R}{R_t} \cdot V_s$$
$$= \frac{3}{10} \cdot 20 = 6v = \text{Answer}$$

► 7v

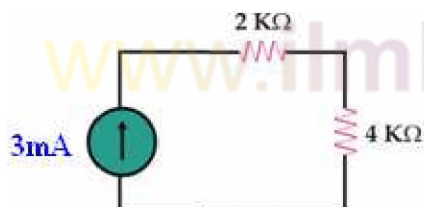**Question No: 5 ( Marks: 1 ) – Please choose one**

In the given series fig. the total voltage of circuit is



► 6V

► 12V


► 18V

$$V = IR$$
$$= 3Ma \cdot 4 + 2 = 3Ma \cdot 6$$
$$= 18V = \text{Ans....}$$

► 10V

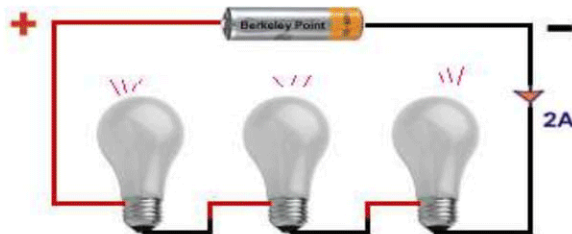**Question No: 6 ( Marks: 1 ) – Please choose one**

In given circuit power dissipated across each bulb is 20w.What would be the resistance of each bulb.



► **5Ω**  $P=V \cdot I$   
 $20 = V \cdot 2A$   
 $20/2 = V$   
 $V=10v$   
So,  
 $R=V/I = 10/2 = 5 \text{ ohm} = \text{Ans.....}$

- 10Ω
- 40Ω
- 20Ω

**Question No: 7 ( Marks: 2 )**

What is the unit of capacitance and Inductance?

**Answer:**

The SI unit of capacitance is the farad; 1 farad = 1 coulomb per volt.  
The unit of inductance is the henry (H) named after American scientist and magnetic researcher Joseph Henry. 1 H = 1 Wb/A

**Question No: 8 ( Marks: 2 )**


Define KIRCHHOFF'S VOLTAGE LAW (KVL):

**Answer:**

Kirchhoff's Voltage Law (or Kirchhoff's Loop Rule) is a result of the electrostatic field being conservative. It states that "the total voltage around a closed loop must be zero". If this were not the case, then when we travel around a closed loop, the voltages would be indefinite. So,  $\sum V=0$

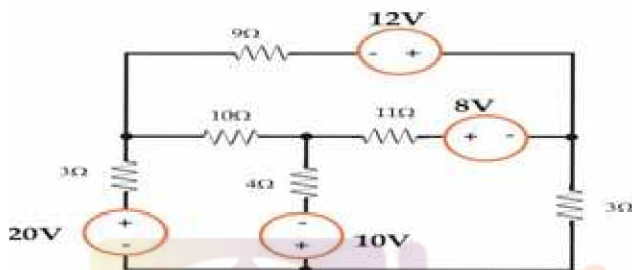
**Question No: 9 ( Marks: 3 )**

Draw and label loop currents for circuit.write kvl for any one loop equation.



**Solution:**

Circuit will be redrawn as

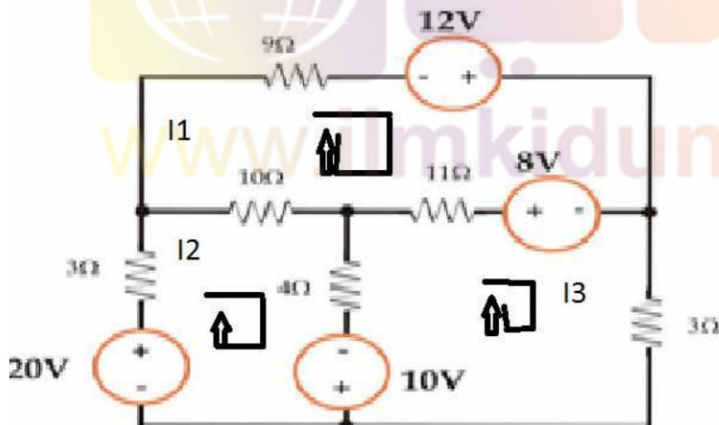


**KVL for loop 1 is**

$$9I_1 + 12 + 8 + 11(I_1 - I_3) + 10(I_1 - I_2) + 9I_1$$

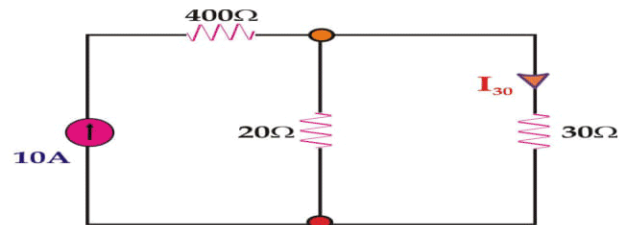**Question No: 10 ( Marks: 5 )**

You are given the circuit Use Current Division Rule directly to find  $I_{30}$ .



**Solution:**

Formula is

$$I_1 = \frac{R_2}{R_1 + R_2}$$

AS we see that 30 ohm is in parallel with 20 ohm, So the resistance will become 12 ohm..

Now,


Using formula, we have

$$\begin{aligned} I_{30} &= \frac{400}{400 + 12} \times 10 \\ &= \frac{4000}{412} \\ &= 9.7 \text{ A} \end{aligned}$$

www.ilmkidunya.com

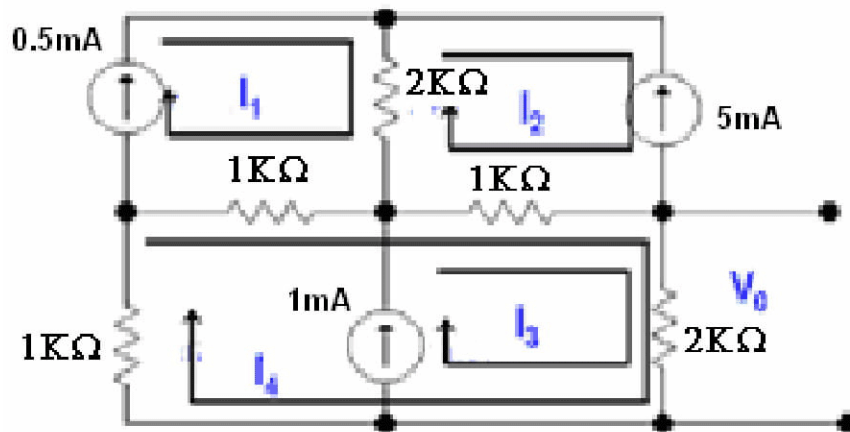Question No: 11 ( Marks: 5 )

Determine the value  $I_4$  for the given network.



**Solution:**

$$I_1 = 0.5mA,$$

$$I_2 = -5mA,$$

$$I_3 = 1mA$$

FOR  $I_4$

$$1k(I_4 - I_1) + 1k(I_4 - I_2) + 1kI_3 + 2kI_3 + 1kI_4 = 0$$

$$= 2kI_4 - 1kI_2 + 3kI_3 = 0$$

PUTTING I VALUES

$$= 2kI_4 - 5 + 3 = 0$$


$$= 2kI_4 - 2 = 0$$

$$= I_4 = \frac{2}{2} = 1mA....$$

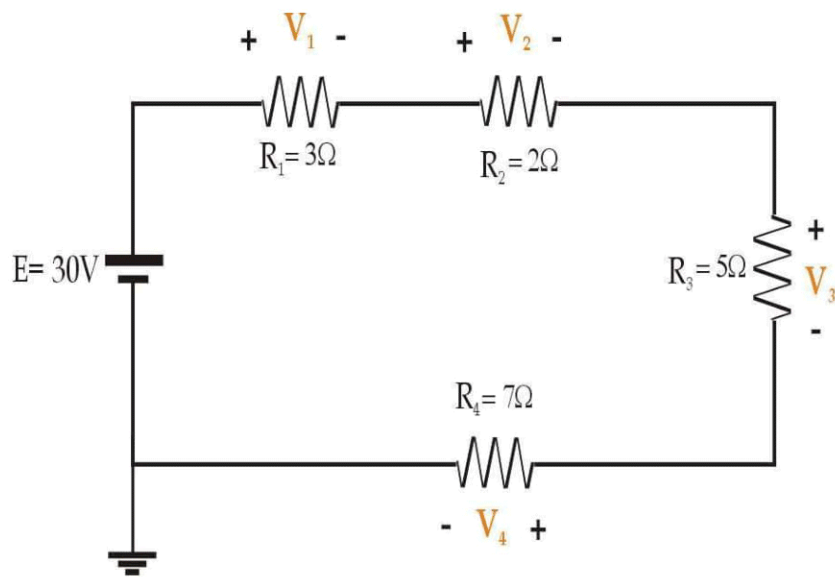**Question No: 12 ( Marks: 10 )**

If 1.76A current is flowing through circuit

Calculate the power dissipated by  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ . Determine the power delivered by the source, Write each step of the calculation to get maximum marks and also mention the units of each derived value.



**Solution:**

$$I = 1.76 \text{ A}$$

As the formula for power delivered by source is

$$P = \frac{V^2}{R}$$

So,

$$P = \frac{30^2}{17} = \frac{900}{17}$$

$$P = 52.94 \text{ Watts}$$

Now Power dissipated in each resistor will:

$$P = I^2 R$$

$$P_1 = (1.76)^2 \times 3$$

$$P_1 = 9.2 \text{ watts}$$

$$P_2 = (1.76)^2 \times 2$$

$$= 6.19 \text{ watts}$$

$$P_3 = (1.76)^2 \times 5$$

$$= 15.48 \text{ watts}$$

$$P_4 = (1.76)^2 \times 7$$

$$= 21.68 \text{ watts}$$